



CPSC3300 – Computer Systems Organization
Homework #2 – Boolean Algebra and Adders
Due: 11:59PM Monday, February 8
Submit to Canvas

Total 100pts

1. [20pts] Logical completeness



- a. Show that you can use only two-input NAND gates to implement each of the following two-input logic functions, and draw the used NAND gates and wiring.

- i. NOR function
- ii. XOR function

  


- b. Show that you can use only two-input NOR gates to implement each of the following two-input logic functions, and draw the used NOR gates and wiring.

- i. NAND function
- ii. XOR function

  

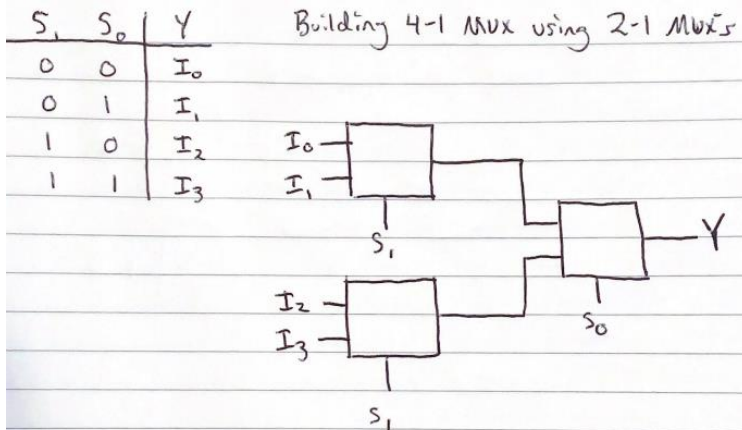2. [10pts] Show how to use 2-1 Muxes to build a 4-1 Mux. Draw the used 2-1 Muxes and the wiring, and mark the 4 inputs and 1 output for the resulting 4-1 Mux.



3. [10pts] Demonstrate by means of truth tables whether the following identities are valid or not:

a. $\overline{A+B+C} = \overline{A} + \overline{B} + \overline{C}$

a. $\overline{A+B+C} = \overline{A} + \overline{B} + \overline{C}$

A	B	C	$A+B+C$	$\overline{A+B+C}$	\overline{A}	\overline{B}	\overline{C}	$\overline{A} + \overline{B} + \overline{C}$
0	0	0	0	1	1	1	1	1
0	0	1	1	0	1	1	0	1
0	1	0	1	0	1	0	1	1
0	1	1	1	0	1	0	0	1
1	0	0	1	0	0	1	1	1
1	0	1	1	0	0	1	0	1
1	1	0	1	0	0	0	1	1
1	1	1	1	0	0	0	0	0

Compare these two columns

Not Equal

b. $A \cdot B + C = (A+C) \cdot (B+C)$

b. $A \cdot B + C = (A+C) \cdot (B+C)$

A	B	C	$A \cdot B$	$(A \cdot B) + C$	$A+C$	$B+C$	$(A+C) \cdot (B+C)$
0	0	0	0	0	0	0	0
0	0	1	0	1	1	1	1
0	1	0	0	0	0	1	0
0	1	1	0	1	1	1	1
1	0	0	0	0	1	0	0
1	0	1	0	1	1	1	1
1	1	0	1	1	1	1	1
1	1	1	1	1	1	1	1

Compare these two columns

TRUE, EQUAL

4. [20pts] Prove the identity of each of the following Boolean equations, using algebraic manipulation:

a. $(\bar{A} + \bar{B}) \cdot (\bar{A} + B) \cdot (A + \bar{B}) = \bar{A} \cdot \bar{B}$

$$a. (\bar{A} + \bar{B}) \cdot (\bar{A} + B) \cdot (A + \bar{B}) = \bar{A} \cdot \bar{B}$$

$$(\bar{A} + \bar{B})(\bar{A} + B)(A + \bar{B}) = \bar{A} \cdot \bar{B}$$

$$\bar{A} \cdot \bar{B} = \bar{A} \cdot \bar{B}$$

b. $\bar{A} \cdot B + \bar{B} \cdot \bar{C} + A \cdot B + \bar{B} \cdot C = 1$

$$b. \bar{A} \cdot B + \bar{B} \cdot \bar{C} + A \cdot B + \bar{B} \cdot C = 1$$

$$\bar{A}B + \bar{B}\bar{C} + AB + \bar{B}C = 1$$

$$\bar{A}B + \bar{B}(\bar{C} + C) + AB = 1$$

$$\bar{A}B + \bar{B} + AB = 1$$

$$\bar{B} + \bar{A}B + AB = 1$$

$$\bar{B}(A + \bar{A}) + \bar{B} = 1$$

$$\bar{B} + \bar{B} = 1$$

$$1 = 1$$

5. [20pts] For the Boolean function O1 and O2, as given in the following truth table:

Input			Output	
x	y	z	O1	O2
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	1

a. List the minterms for a three-variable function with variables x, y, and z.

$$a. \text{ minterms: } O_1 = (x \cdot z) + (\bar{x} \cdot y) + (\bar{x} \cdot \bar{z})$$


$$O_2 = (x \cdot y) + (x \cdot \bar{z}) + (\bar{x} \cdot \bar{y} \cdot z)$$

- b. Express O1 and O2 in sum-of-product algebraic form.

$$O_1 = \bar{x} \cdot \bar{y} \cdot \bar{z} + \bar{x} \cdot y \cdot \bar{z} + \bar{x} \cdot y \cdot z + x \cdot \bar{y} \cdot \bar{z} + x \cdot y \cdot \bar{z}$$

$$O_2 = \bar{x} \cdot \bar{y} \cdot z + x \cdot \bar{y} \cdot \bar{z} + x \cdot y \cdot \bar{z} + x \cdot y \cdot z$$

 6. [20pts] In class, we learned the implementation for a 4-bit carry lookahead adder. We can use the same idea and extend to build a 16-bit carry lookahead adder. Denote this implementation as a one-level carry lookahead adder.
- In the textbook, Figure 8.6.3 shows a two-level implementation of a 16-bit carry lookahead adder. This adder uses 4-bit carry lookahead adders at the lower level, and uses a carry lookahead unit at the higher level.
- Compare these two implementations and provide your explanation why the two-level implementation could be preferred.



A one-level carry lookahead adder can compute 4 bits across gates with $n/4$ blocks and a high number of gate delays. Information can take longer to process using just one level carry lookahead adders, but with the advanced computing speed when you move to a two-level carry lookahead adder that can implement with 16 bits, the speed increases tremendously. For example, a one-level carry lookahead adder for 4-bits would have a total of 6 gate delays, while a basic two-level adder processing 64 bits would have a total of 14 gate delays while processing much more information.